# **Electrical Systems Knowledge Organiser – Year 6**

## **Complex Circuits and Switches**

#### Switches and sensors



Latchin switch



Push-to-make switch
When you push, the electricity
flows through the circuit, but
when you release it the circuit is
broken and the switch is off.




Push-to-break switch
The switch is off while the button
is pushed, but returns to its 'on'
position when button is released.



Light-dependent p-switch resistor (LDR)

- Micro-switch a switch that can operate as push-to-break switch or a push-to-make switch.
- Push-to-break switch a switch turned off by pressing it.
- Push-to-make switch a switch turned on by pressing it.
- Reed switch a switch operated by a magnet.
- Tilt switch a switch that works when tilted at an angle.
- Toggle switch a switch operated when a lever is pressed.
- Light dependent resistor (LDR) a sensor that operates when light is shined on it.

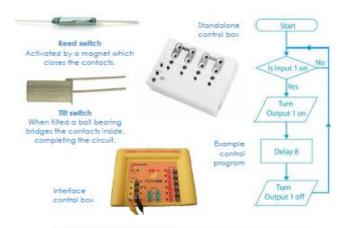



# Engineer Study Sir Jony Ive

- ✓ Sir Jonathan Paul Ive, is a British industrial designer and Apple executive who was responsible for making design as integral to the appeal of a personal computer as its power and speed.
- ✓ He is responsible for the design of many Apple products we use today such as the iMac, iPhone, ipad and iWatch.



## Vocabulary

**Series circuit:** all components are connected end-to-end to form a single path for current flow.

Parallel circuit: an electrical path that branches so that the current divides and only part of it flows through any branch.

**Open switch:** when a switch is positioned such that electricity cannot flow through it.

Closed switch: when a switch is positioned such that electricity can flow through it.

Output devices: components that produce an outcome e.g. bulbs and buzzers.

**Input devices:** components that are used to control an electrical circuit e.g. switches or sensors.